
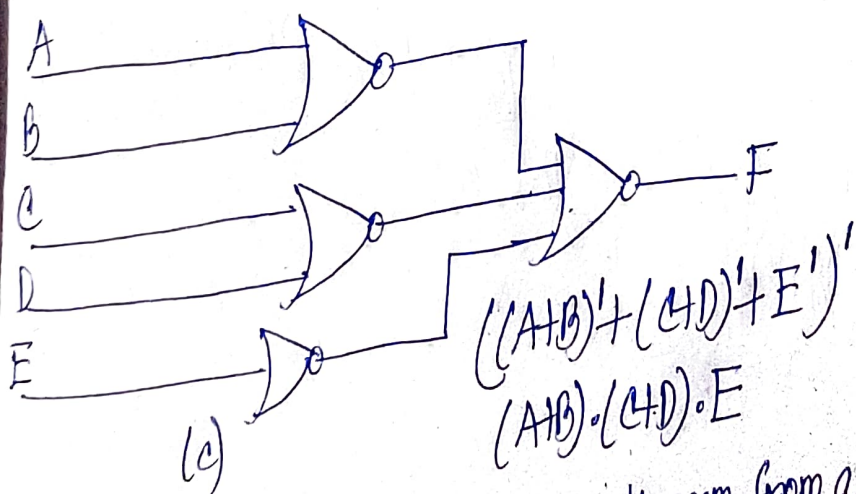
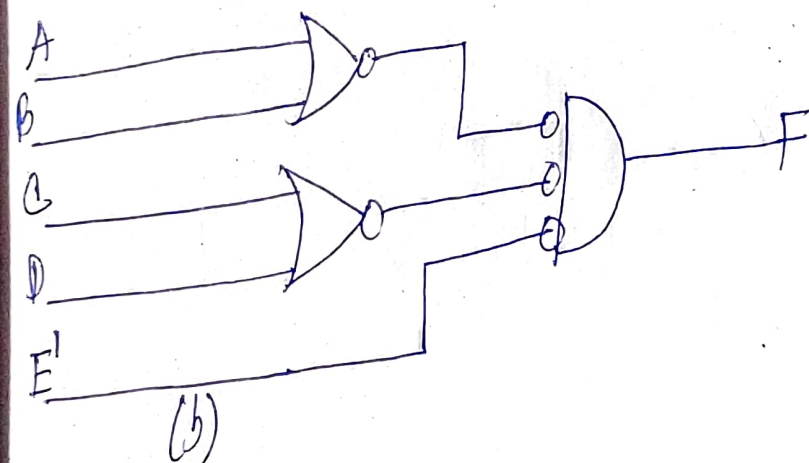


• The implementation of a Boolean function with NOR gates requires that the function be simplified in product of sums form.

Example: $F = (A+B)(C+D)E$

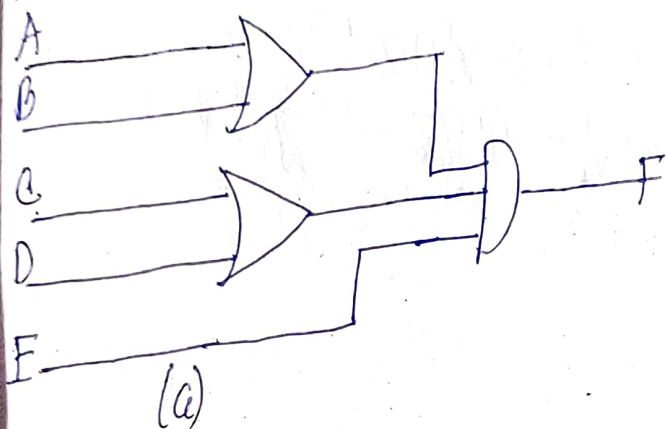

The rule for obtaining the NOR logic diagram from a Boolean function can be derived from this transformation. It is similar to the three-step NAND rule, except that the simplified expression must be in the POS and the terms for the first-level NOR gates are the sum terms. A term with a single literal requires a one-input NOR or inverter gate or may be