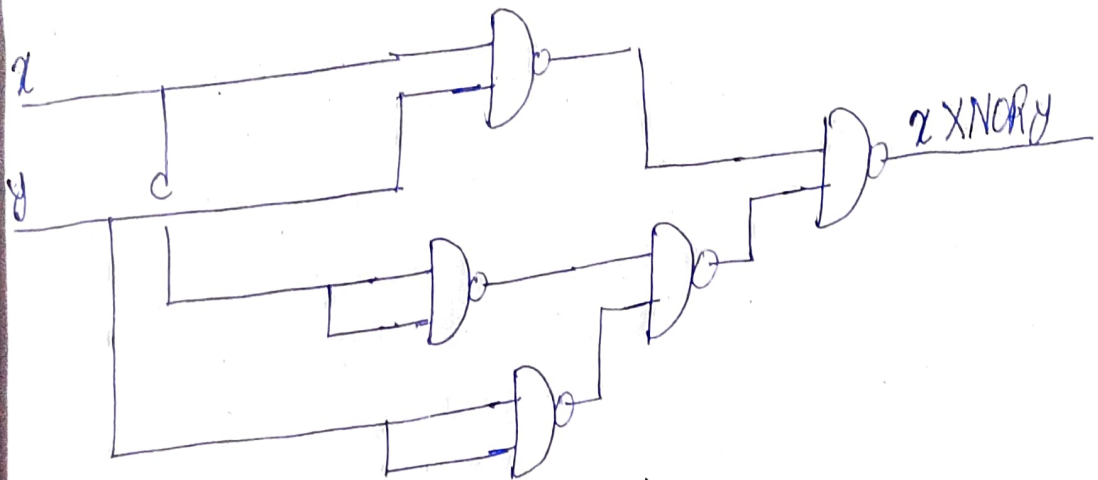



2-25: Implement Ex-NOR gate using minimum number of NAND gate and NAND gates using minimum number of NOR gates.

Solution: The Boolean expression of XNOR gate is $x \cdot y + x' \cdot y'$.

$$\begin{aligned} x \cdot y + x' \cdot y' &= ((x \cdot y + x' \cdot y'))' \quad (\text{Theorem 3}) \\ &= ((x \cdot y)' \cdot (x' \cdot y')')' \quad (\text{Theorem 5(a)}) \\ &= ((x \cdot y)' \cdot ((x \cdot x')' \cdot (y \cdot y')'))' \quad (\text{Theorem 1(b)}) \\ &= ((x \text{ NAND } y) \text{ NAND } ((x \text{ NAND } x) \text{ NAND } (y \text{ NAND } y)))' \end{aligned}$$


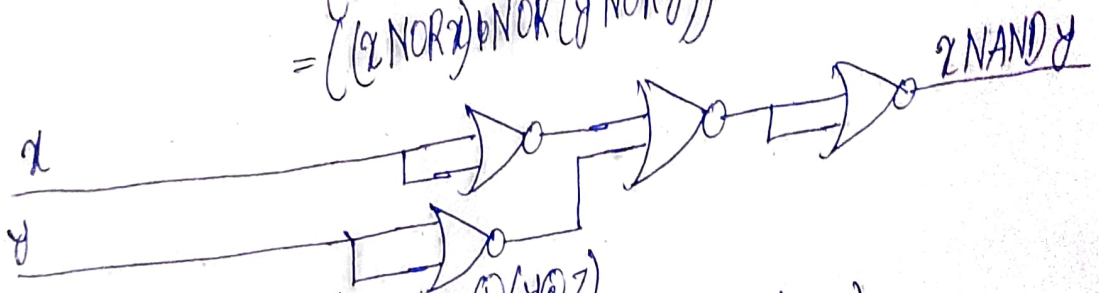
$$\begin{aligned} x \text{ NAND } y &= (x \cdot y)' = x' + y' \quad (\text{Theorem 5(b)}) \\ &= ((x' + y')')' \quad (\text{Theorem 3}) \\ &= ((x' + y')' + (x' + y')')' \quad (\text{Theorem 1(a)}) \\ &= ((x \text{ NOR } x) \text{ NOR } (y \text{ NOR } y))' \end{aligned}$$



2-26: Show that $(x \oplus y) \odot z = x \oplus (y \odot z)$

x	y	z	$x \oplus y$	$(x \oplus y) \odot z$	$y \odot z$	$x \oplus (y \odot z)$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	1	1	0	1
0	1	1	1	0	1	1
1	0	0	1	1	0	1
1	0	1	1	0	0	1
1	1	0	0	0	1	0
1	1	1	0	1	1	0