


2-9: Obtain the truth table of the function:

$$F = xy + xy' + y'z$$


x	y	z	xy	xy'	xy'	y'z	xy + xy' + y'z
0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0
0	1	0	0	0	0	0	0
0	1	1	0	0	0	0	0
1	0	0	0	1	1	0	1
1	0	1	0	1	1	0	1
1	1	0	1	0	0	0	1
1	1	1	1	0	0	0	1

2-10: Implement the simplified Boolean functions from problem 2-6 with logic gates.


a) $A'B' + B \cdot (A+C)$

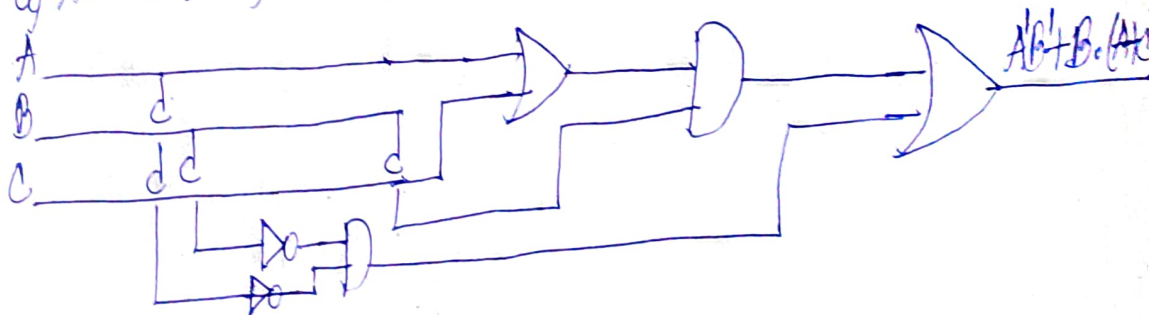

b) $BC + AC'$

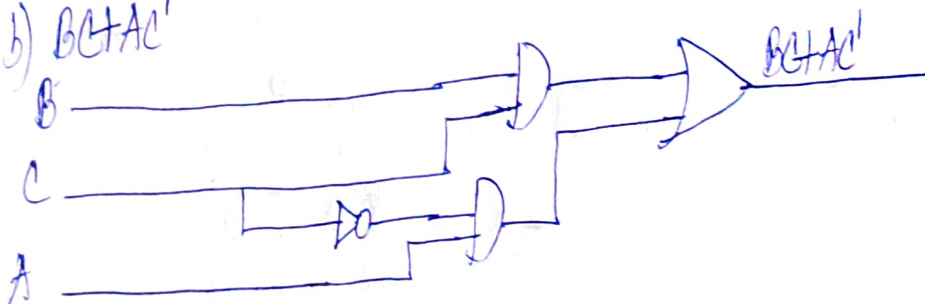

c) $CD + A$

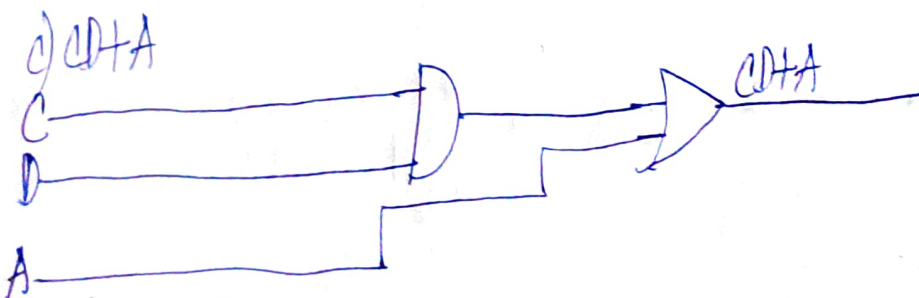

d) $(A+C)(A+B')$